
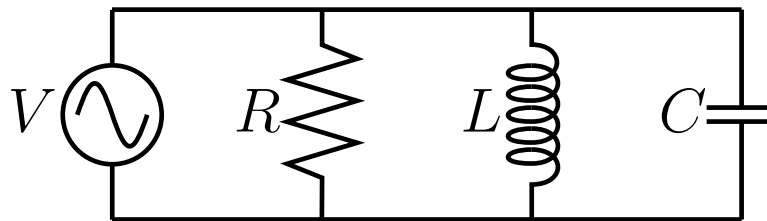


Tutorial 15 Question

- Ch 31: Pr. 48 (revised).
- A resistor R , capacitor C , and inductor L are connected in parallel across an ac generator as shown below. The source emf is $V = V_0 \sin \omega t$. Determine the current as a function of time (including amplitude and phase) (a) in the resistor, (b) in the inductor, (c) in the capacitor. (d) What is the total current leaving the source? (Give amplitude I_0 and phase.) (e) Determine the impedance Z defined as $Z = V_0/I_0$. (*Bonus*) What is the power factor?

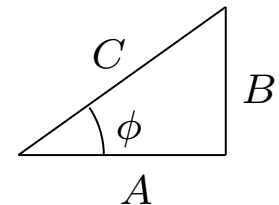

- Hint: $C \sin(x + \phi) = A \sin x + B \cos x$ looks like



Solution

- (a) Determine the current in the resistor.
- From Kirchhoff's loop rule the voltage across the resistor is $V = V_0 \sin \omega t$.
 - The current is in phase with voltage in resistors, so $I_R = I_{R,0} \sin \omega t$.
 - Ohm's law tells us $I_{R,0} = V_0/R$ so

$$I_R(t) = \frac{V_0}{R} \sin \omega t.$$

Solution, contd

(b) Determine the current in the inductor.

- Again, the voltage drop is V . But this time the voltage leads the current by $\phi = 90^\circ$ (CIVIL) so

$$I_L = I_{L,0} \sin \left(\omega t - \frac{\pi}{2} \right) = -I_{L,0} \cos \omega t.$$

- The current amplitude is related to the voltage by reactance, $I_{L,0} = V_0/X_L$ so

$$I_L(t) = -\frac{V_0}{X_L} \cos \omega t.$$

- (Note: $X_L = \omega L$.)



Solution, contd

(c) Determine the current in the capacitor.

- Same V . Now the current leads by $\phi = 90^\circ$ (CIVIL) so

$$I_C = I_{C,0} \sin\left(\omega t + \frac{\pi}{2}\right) = I_{C,0} \cos \omega t.$$

- Again, the amplitude is given by reactance, $I_{C,0} = V_0/X_C$ so

$$I_C(t) = \frac{V_0}{X_C} \cos \omega t.$$

- (Note: $X_C = \frac{1}{\omega C}$.)



Solution, contd

(d) What is the total current leaving the source?

- The total current I splits (Kirchhoff's branch rule) so

$$I = I_R + I_L + I_C = I_{R,0} \sin \omega t + (I_{C,0} - I_{L,0}) \cos \omega t.$$

- To equate this to $I = I_0 \sin(\omega t + \phi)$ we use the hint. The amplitude is

$$\begin{aligned} I_0 &= \sqrt{I_{R,0}^2 + (I_{C,0} - I_{L,0})^2} \\ &= V_0 \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}. \end{aligned}$$

- Let's wait with determining the phase ϕ until we've found the impedance Z .



Solution, contd

(e) Determine the impedance Z .

• If $Z = V_0/I_0$ then

$$Z = \left[\frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L} \right)^2 \right]^{-\frac{1}{2}}.$$

• Notice how this is similar (but not identical, because of the squared powers) to the formula for parallel resistors,

$$\frac{1}{Z^2} = \frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L} \right)^2.$$

• Also notice that $Z \leq R$, always.

Solution, contd

(d) contd

- Now we can write down the current's phase in a more familiar form,

$$\cos \phi = \frac{I_{R,0}}{I_0} = \frac{V_0/R}{V_0/Z} = \frac{Z}{R}.$$

- Weird, that's the inverse of what we got for series LRC circuits.

(*Bonus*) What is the power factor?

- The power factor is the ratio

$$\text{Power factor} = \frac{\bar{P}}{I_{\text{RMS}} V_{\text{RMS}}}.$$



Solution, contd

(*Bonus*) contd

- The average power (lost through the resistor) is given by

$$\overline{P} = \frac{V_{\text{RMS}}^2}{R}.$$

- From part (d) we get $R = \frac{Z}{\cos \phi}$ so

$$\overline{P} = \frac{V_{\text{RMS}}}{Z} V_{\text{RMS}} \cos \phi.$$

- Since $I_{\text{RMS}} = V_{\text{RMS}}/Z$ we find

$$\overline{P} = I_{\text{RMS}} V_{\text{RMS}} \cos \phi.$$

- So the power factor is still $\cos \phi$ (same as series). □

